

COL216

Computer Architecture

Processor design -
A simple datapath
25th February, 2016

Outline of this lecture

Build the datapath step by step as follows

- Start with some instructions
- Include other instructions one by one
- Identify control signals
- Interconnect datapath and controller

Design of controller in the next class

Instruction subset for implementation

- Data processing (DP) instructions
 - add/sub, logical, test, move
- Data Transfer (DT) instructions
 - ldr, str, ldrb, strb
- Branch instructions
 - b, bl
- Multiply instruction
 - mul


Instruction codes

DP I = 0	4	1	1	1	4	1	4	4	5	2	1	4
	cond	0	0	I	opc	S	Rn	Rd	s_amt	s_typ	0	Rm
DP I = 1	4	1	1	1	4	1	4	4	4	8		
	cond	0	0	I	opc	S	Rn	Rd	rot	Imm		
mul A = 0	4	6				1	1	4	4	4	4	4
	cond	0 0 0 0 0 0				A	S	Rn	Rd	Rs	1 0 0 1	Rm
DT I = 0 P = 1 W = 0	4	1	1	6			4	4	12			
	cond	0	1	I P U B W L			Rn	Rd	offset			
b bl	4	1	1	1	1	24						
	cond	1	0	1	L	offset						


Actions for DP instructions

- fetch instruction
- access the register file
- pass operands to ALU
- pass result to register file
- increment PC


Fetching instruction

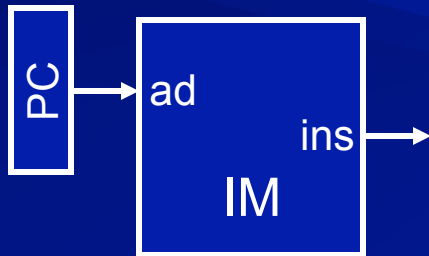


Accessing RF

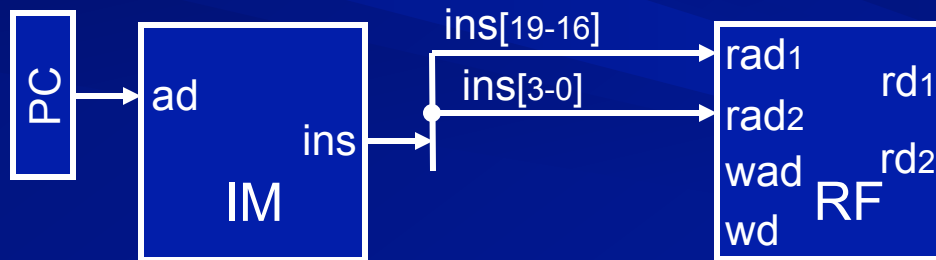


Passing operands to ALU

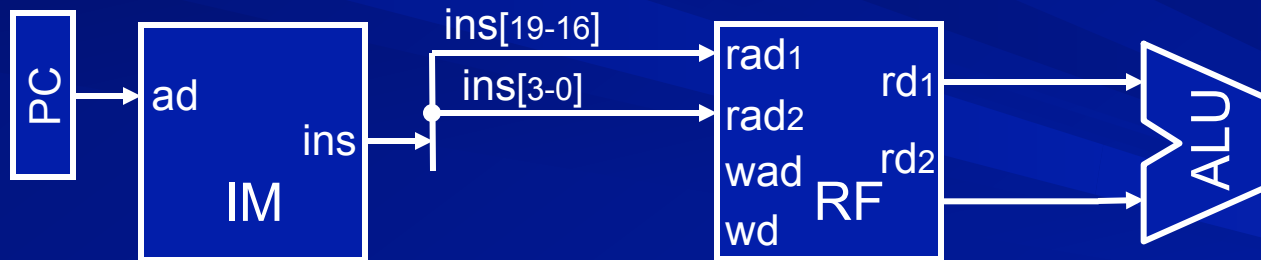

Passing the result to RF

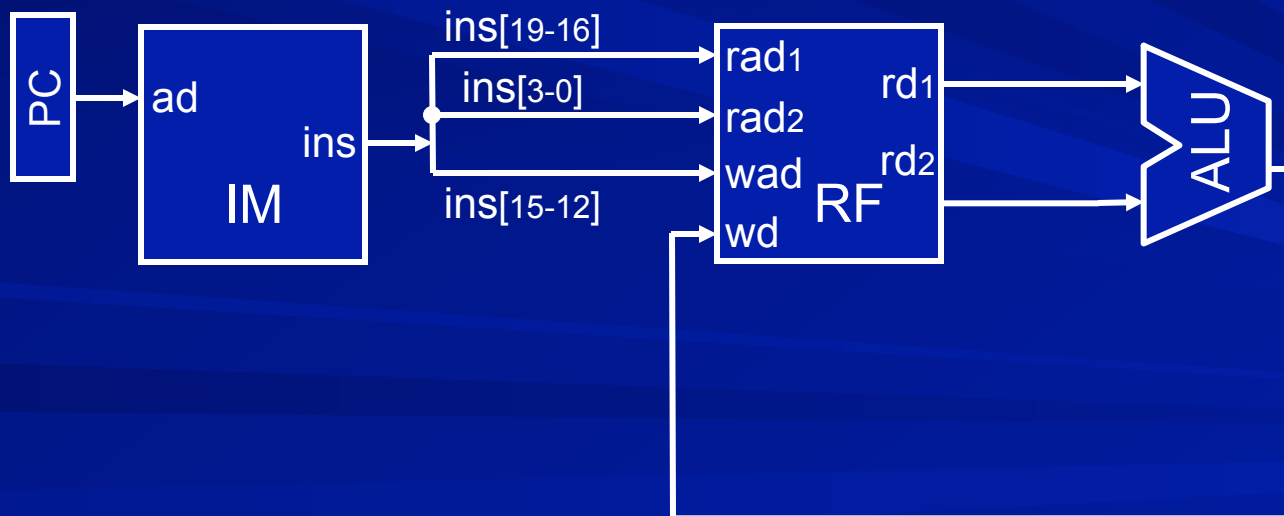


Incrementing PC

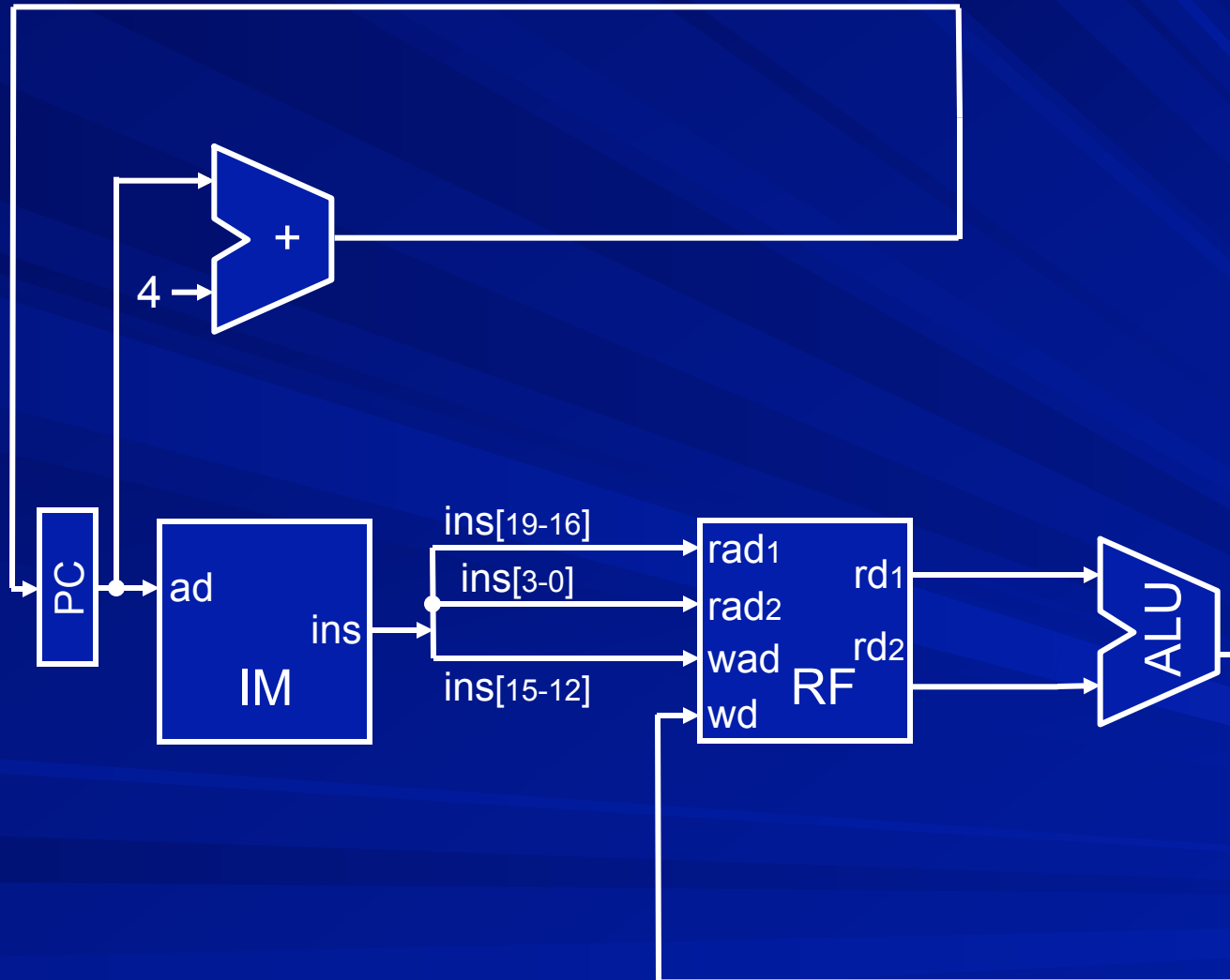

Actions for str instructions

- fetch instruction
- access the register file
- compute address in ALU
- write data into memory
- increment PC


Adding “str” instruction

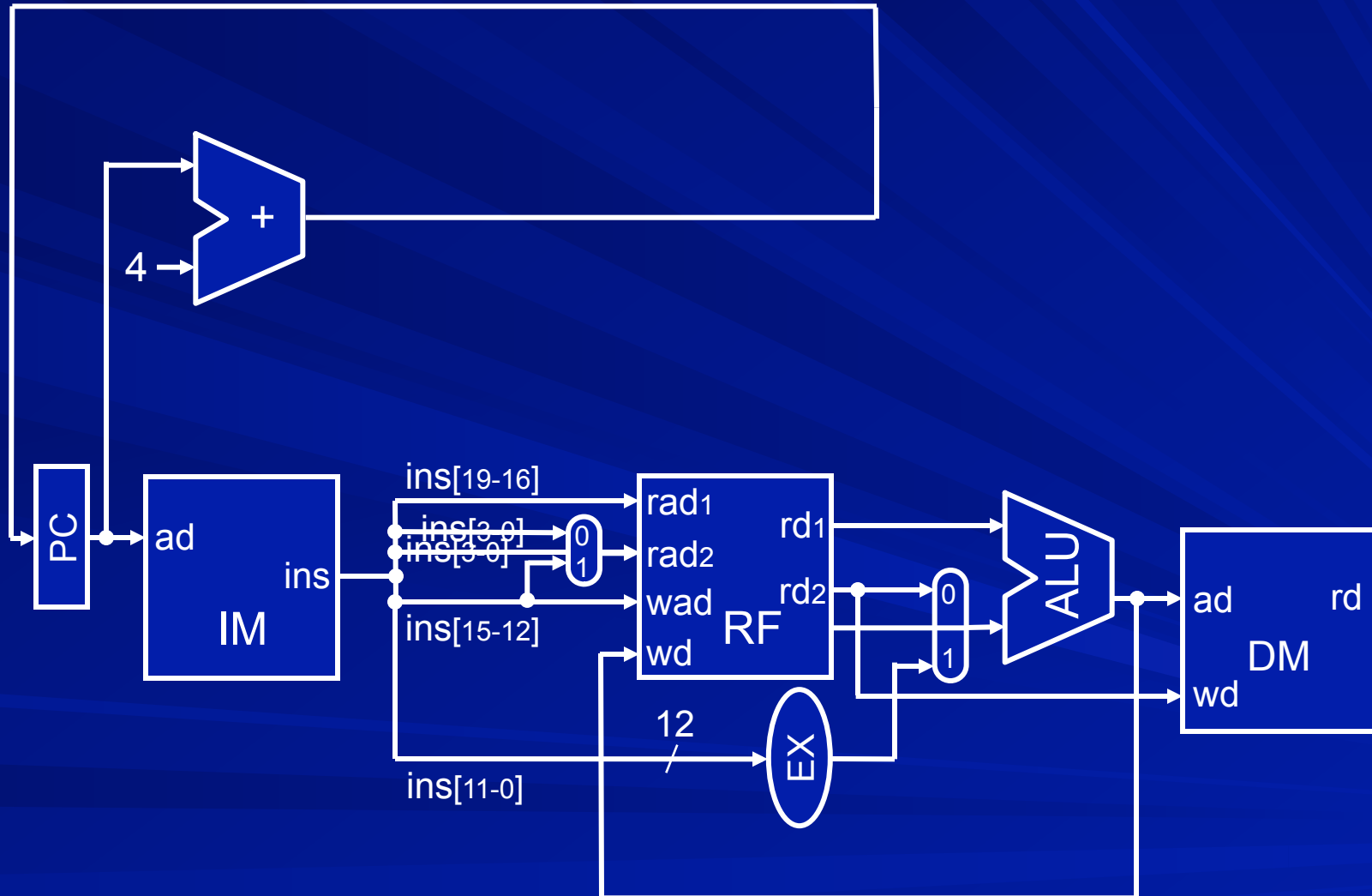

Actions for ldr instructions

- fetch instruction
- access the register file
- compute address in ALU
- read data from memory
- put data in register file
- increment PC


Adding “ldr” instruction

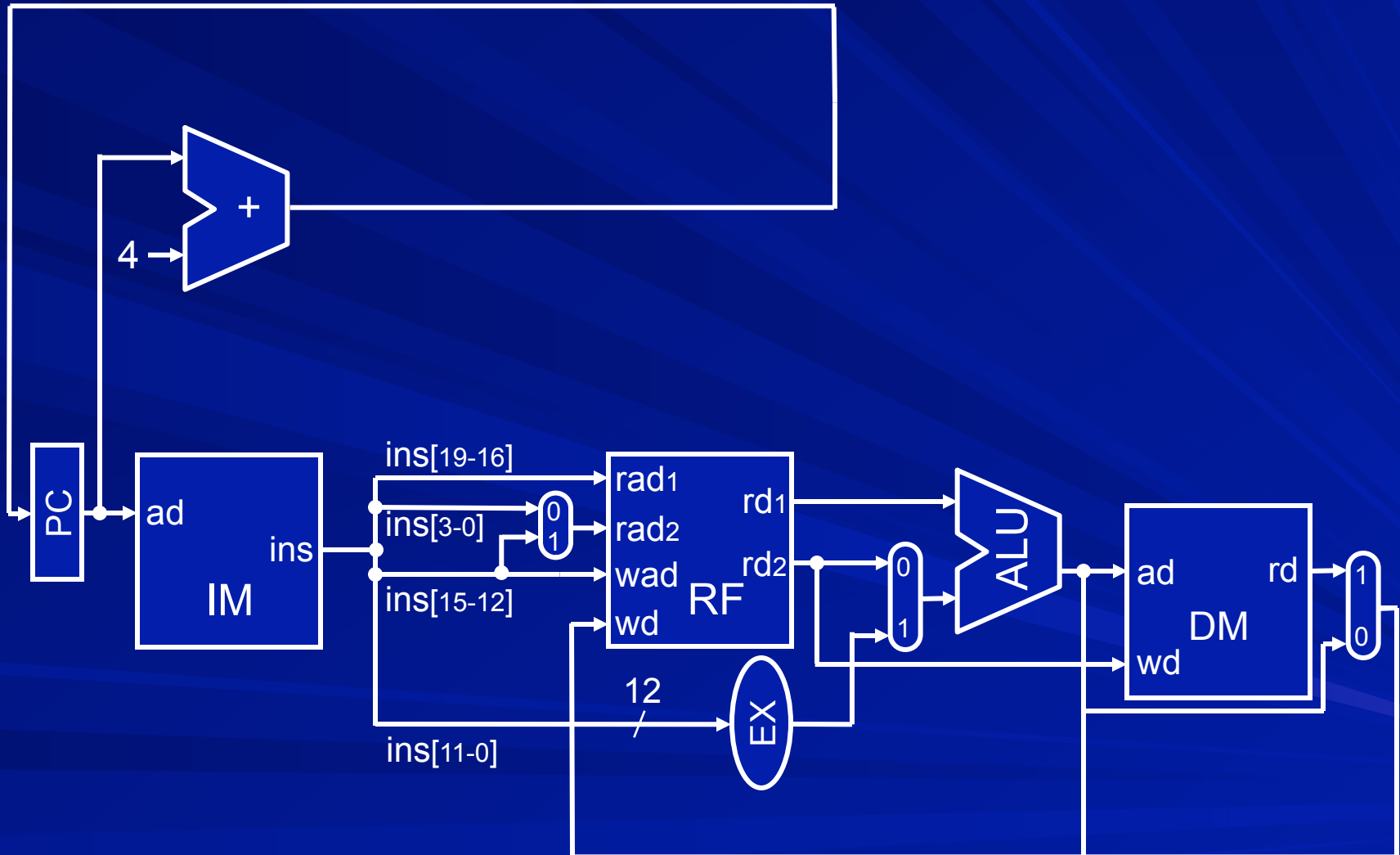




Actions for branch instruction

- fetch instruction
- compute target address
- transfer address to pc


Adding “b” instruction

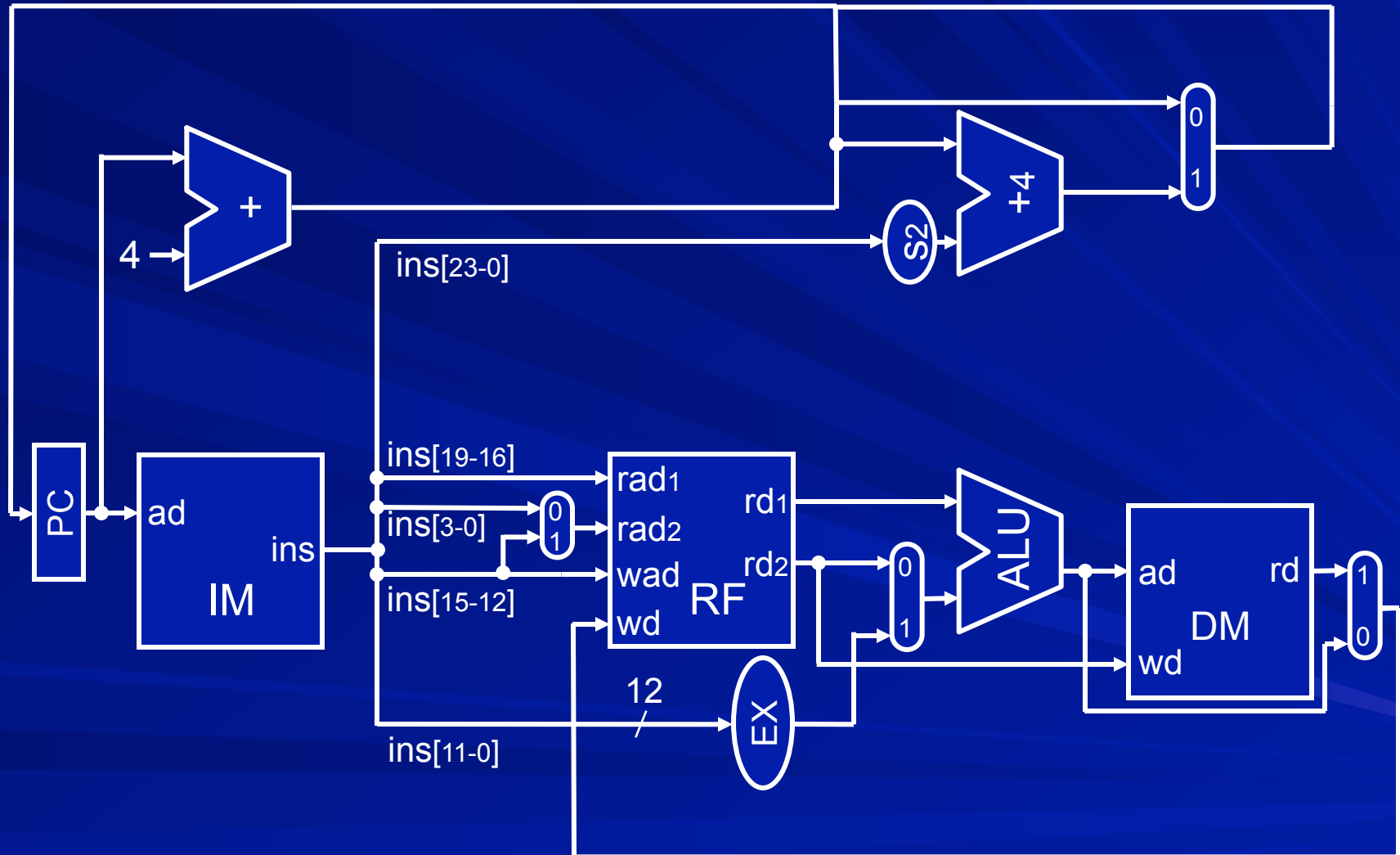


Extending offsets

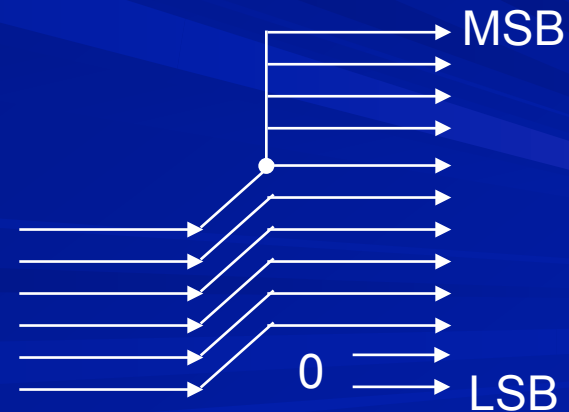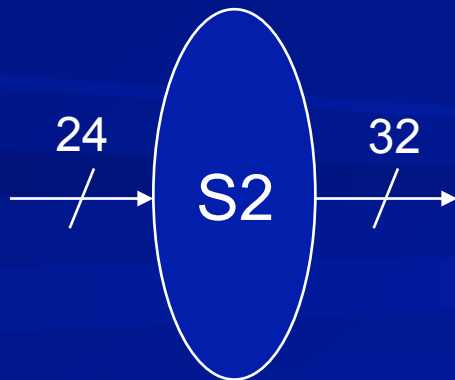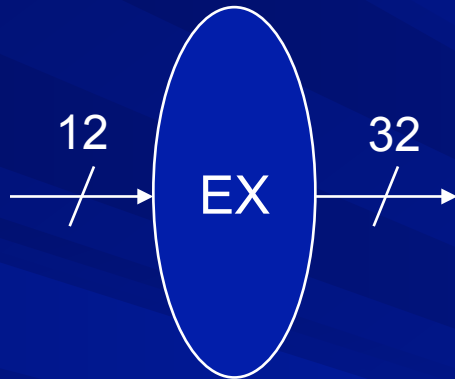

Control Signals

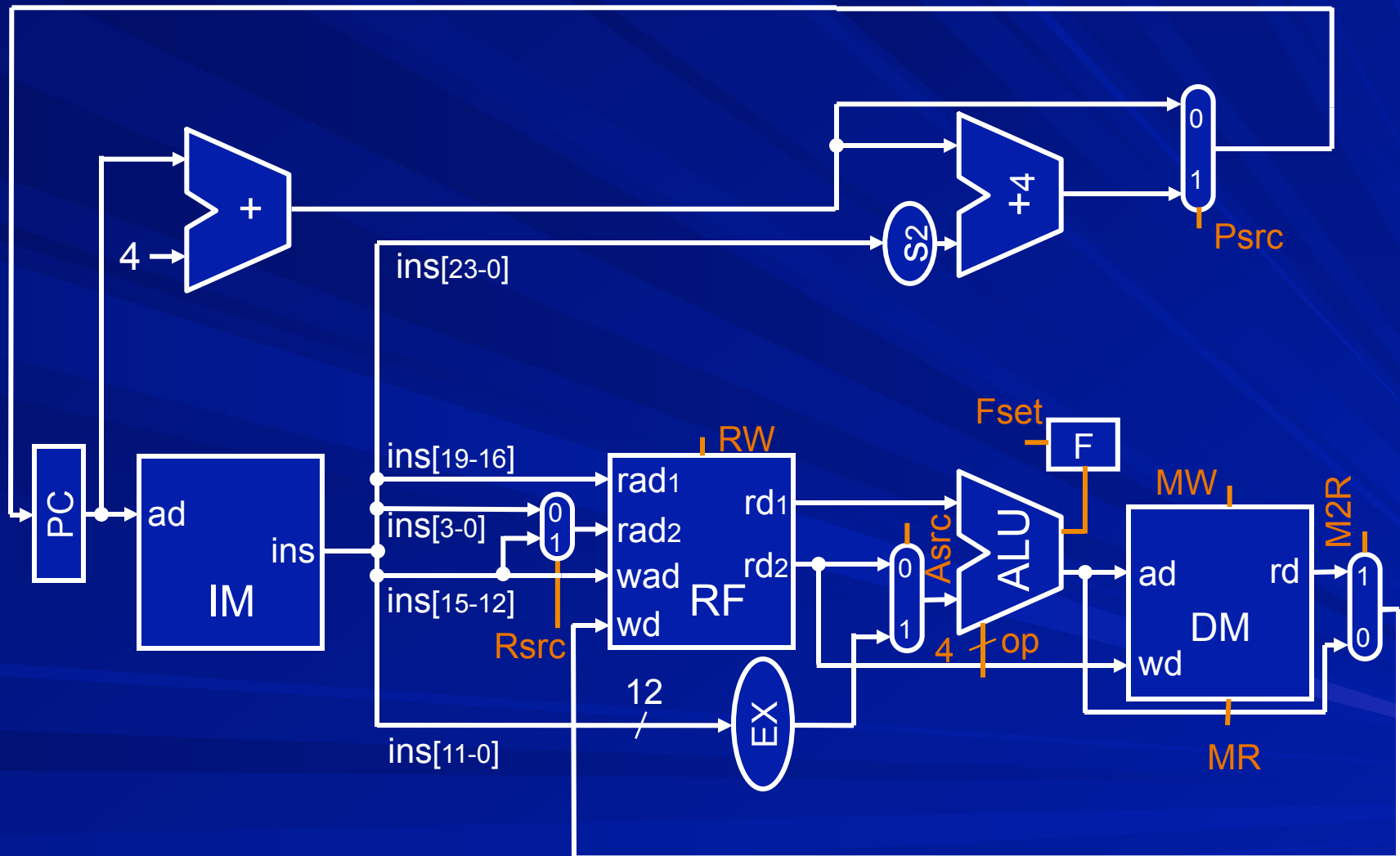

Datapath + Control

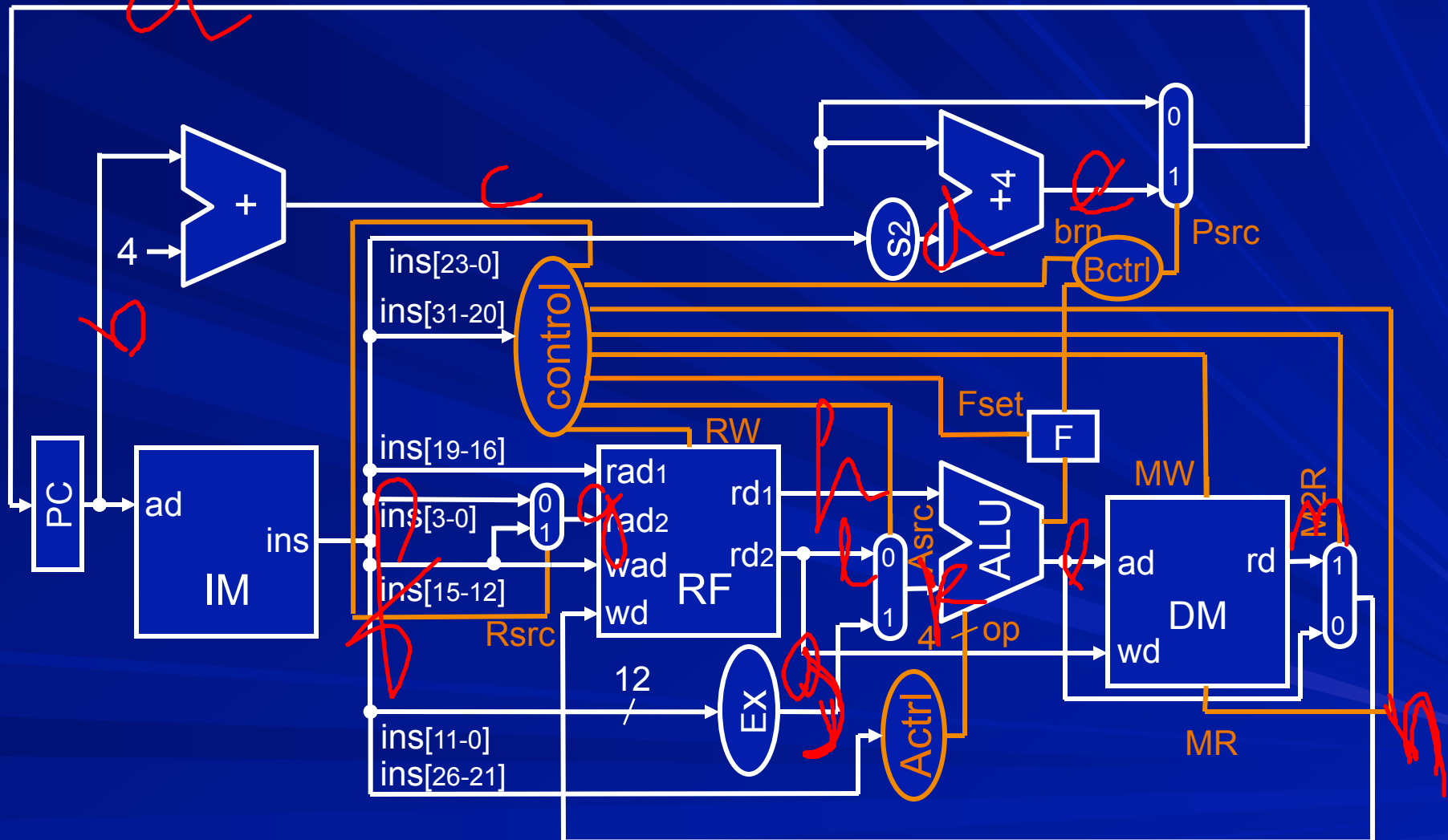

Summary

Processor designed for a small ARM subset

- Step by step approach
- Started with DP instructions
- Added DT, then added branch
- Identified control signals and connected to a controller (black box).