

COL216

Computer Architecture

Divider Design

8th February, 2016

Outline of this lecture

- Division example
- Basic division algorithm
- Proof of correctness
- Circuit design
- Improvements

Division: example

		<u>0011</u>	← Q
0100		00001101	← A
↑		<u>0000000</u>	← 0 x B x 2 ³
B		00001101	
		<u>000000</u>	← 0 x B x 2 ²
		00001101	
		<u>01000</u>	← 1 x B x 2 ¹
		00000101	
		<u>0100</u>	← 1 x B x 2 ⁰
		00000001	← R

Unsigned Division

$$A = Q \times B + R$$

```
step1: i = 0; R = A; Q = 0; D = B
do {
  step2:
    if ( $D \times 2^{n-i-1} \leq R$ )  $R = R - D \times 2^{n-i-1}$  ;  $Q_{n-i-1} = 1$ 
    else  $Q_{n-i-1} = 0$ 
    i ++
} while (i < n)
```

Correctness check

Loop invariant : $A = Q \times D + R$ and $0 \leq R < B \times 2^{n-i}$

At the end of the program, i has a value = n
and D is still = B

For $i = n$, the loop invariant $\Rightarrow 0 \leq R < B$

Therefore R is the correct remainder and Q is
the correct quotient

Base case

Loop invariant : $A = Q \times D + R$ and $0 \leq R < B \times 2^{n-i}$

step1: $i = 0$; $R = A$; $Q = 0$; $D = B$

This ensures the truth of the loop invariant initially, provided $A < B \times 2^n$

This condition is met if we assume that $B \neq 0$ and A is contained within n bits.

Induction over i (case 1)

Loop invariant : $A = Q \times D + R$ and $0 \leq R < B \times 2^{n-i}$

Assume invariant holds before iteration i and
 $D \times 2^{n-i-1} \leq R$

New value of $Q \times D + R$ is

$$(Q + 2^{n-i-1}) \times D + R - D \times 2^{n-i-1} = Q \times D + R$$

The condition of subtraction ensures that

$$D \times 2^{n-i-1} \leq R < D \times 2^{n-i},$$

\therefore after subtraction, $0 \leq R < D \times 2^{n-i-1} = B \times 2^{n-i-1}$

i now becomes $i' = i+1$, $\therefore 0 \leq R < B \times 2^{n-i'}$

Induction over i (case 2)

Loop invariant : $A = Q \times D + R$ and $0 \leq R < B \times 2^{n-i}$

Assume invariant holds before iteration i and
 $D \times 2^{n-i-1} > R$

New value of $Q \times D + R$ is

$$(Q + 0) \times D + R = Q \times D + R$$

The condition of omitting subtraction ensures
that $0 \leq R < D \times 2^{n-i-1}$

Therefore, $i' = i+1$, $0 \leq R < B \times 2^{n-i'}$

Unsigned Division

$$A = Q \times B + R$$

step1: $i = 0$; $R = A$; $Q = 0$; $D = B$

do {

 step2:

 if ($D \times 2^{n-i-1} \leq R$) $R = R - D \times 2^{n-i-1}$; $Q_{n-i-1} = 1$

 else $Q_{n-i-1} = 0$

$i++$

 } while ($i < n$)

can this be avoided ?




Introducing shift registers

$$A = Q \times B + R$$

```
step1: i = 0; R = A; Q = 0; D = B x 2n-1
do {
  step2:
    if (D ≤ R) R = R - D; Q = 2 x Q + 1
    else Q = 2 x Q
    D = D / 2; i ++
} while (i < n)
```

Divider design - 1

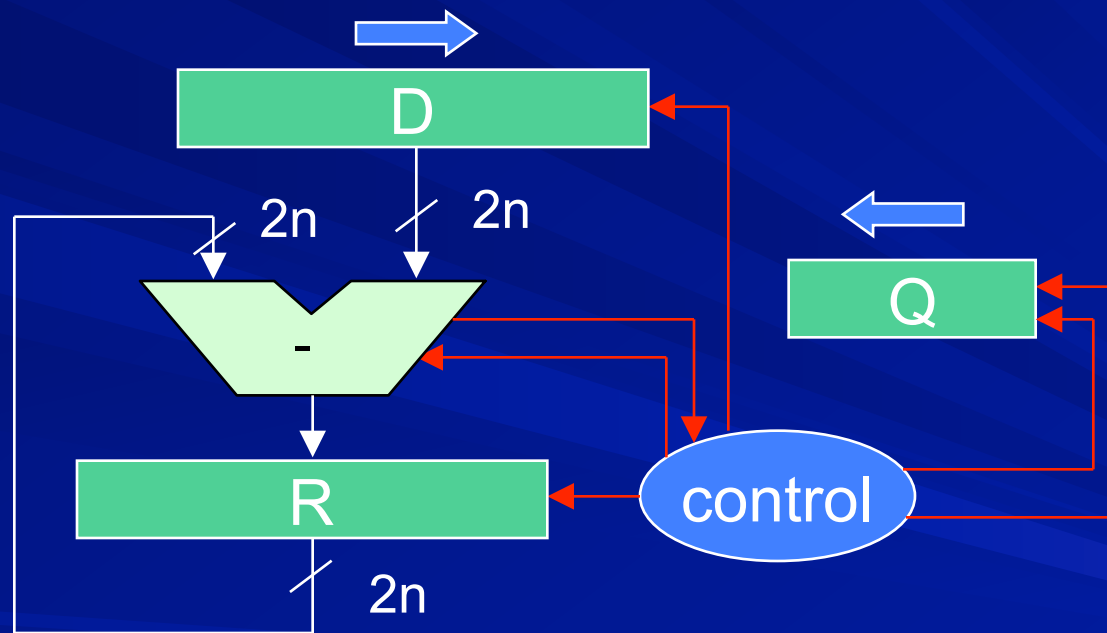

Reducing subtractor size

$$A = Q \times B + R$$

step1: $i = 0$; $R = A$; $Q = 0$; $D = B$

do {

 step2:

$R = 2 \times R$


 if ($D \leq R_H$) $R_H = R_H - D$; $Q = 2 \times Q + 1$

 else $Q = 2 \times Q$


$i++$

} while ($i < n$)

Division: example

 

Divider design - 2

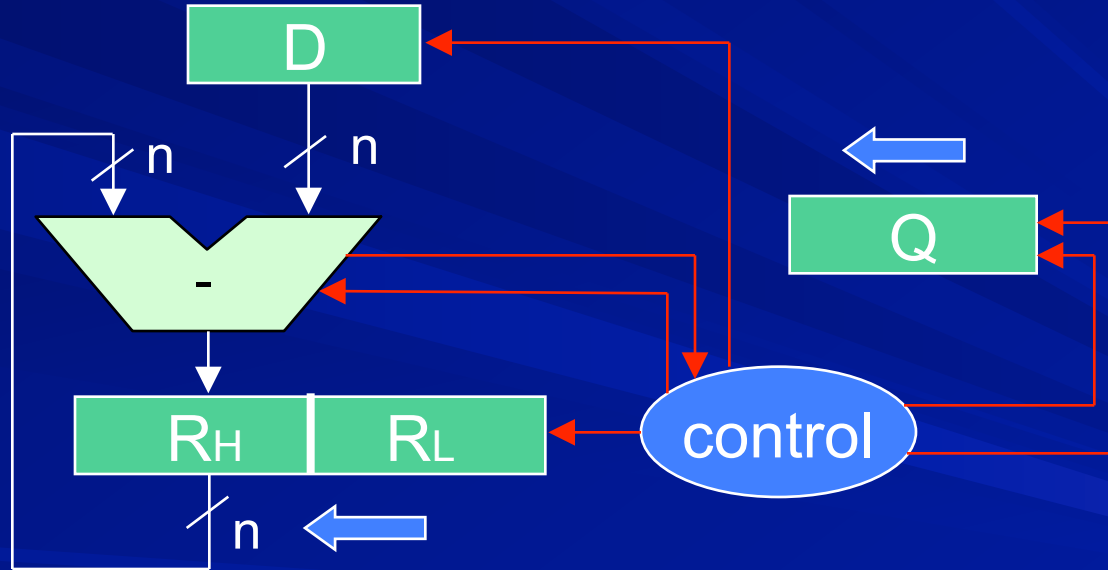

Reducing registers

$$A = Q \times B + R$$

step1: $i = 0$; $R = A$; $D = B$

do {

 step2:

$R = 2 \times R$

 if ($D \leq R_H$) $R_H = R_H - D$; $R = R + 1$

$i++$

} while ($i < n$) # R_H = remainder, R_L = quotient

Divider design - 3

